

Transmission Lines

We have studied wave propagation in unbounded media → media of infinite extent.

Unguided wave propagation → uniform plane wave exists throughout all space and E.M. energy associated → spreads over a wide area.


Wave propagation in unbounded media → radio or TV broadcasting

not useful in situations like telephone connections

Another means of transmitting power or information → Guided structures

↳ ~~Serve~~ to direct the propagation energy from the source to the load.

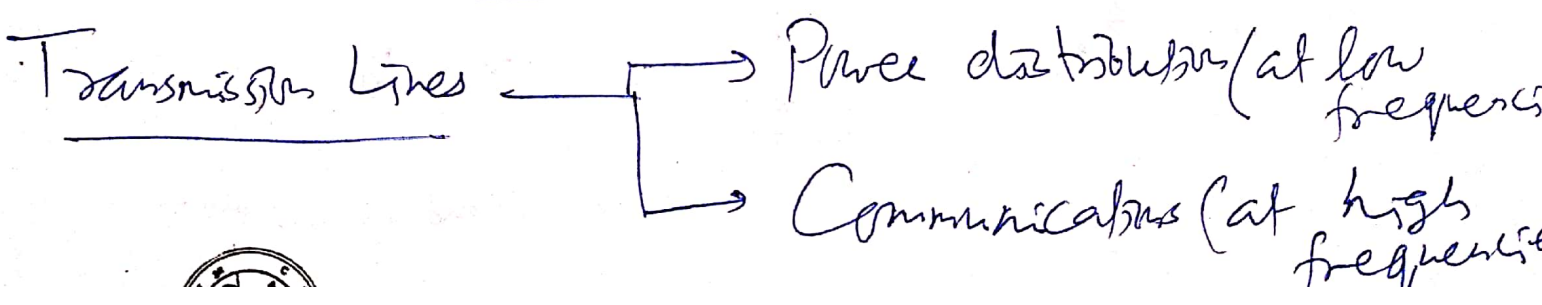Examples → Transmission Lines and Waveguides




Transmission lines → twisted pair and coaxial cables
(thinnet & thicknet)
→ used in computer networks → Ethernet and internet

Transmission Line → consists of two or more parallel conductors used to connect a source to a load

<u>Ex:</u>	Sources	Load
	Hydroelectric generator	Factory
	Transmitter	Antenna
	Oscillator	Oscilloscope

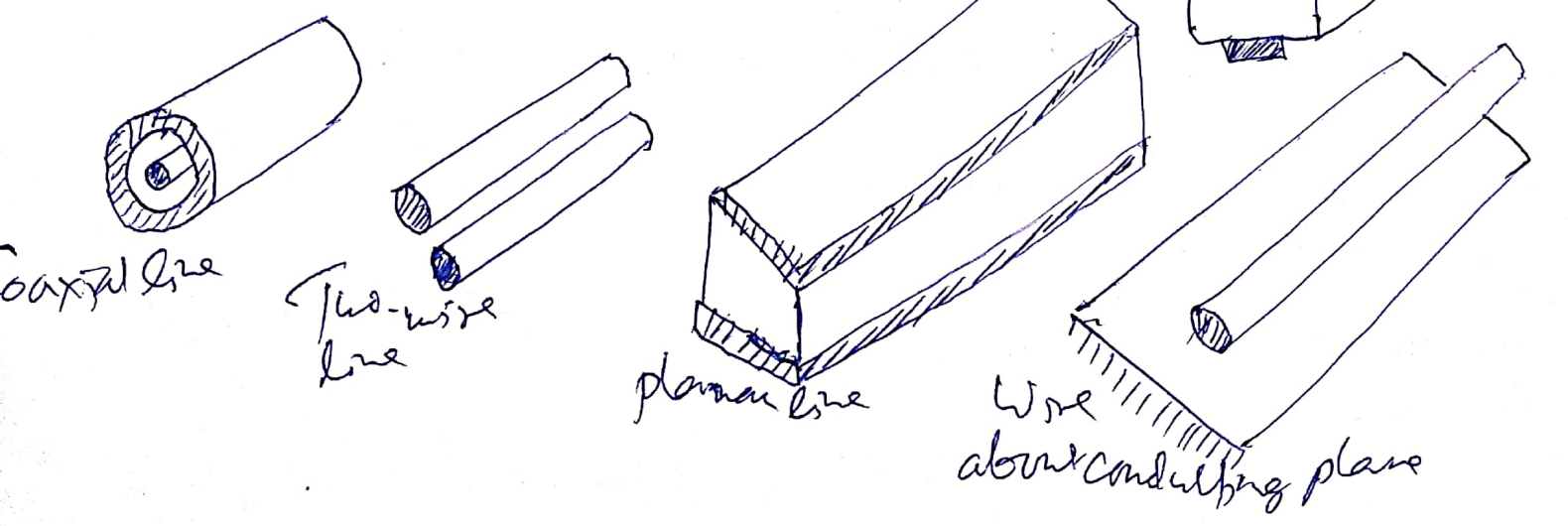Transmission lines include → coaxial cable, a two-wire line, a parallel plate or planar line, a wire above the conducting plane and a microstrip line.



Coaxial cables → used in electrical laboratories (25)

Microstrip lines → Important in integrated circuits
→ metallic strips connecting electronic elements are deposited in dielectric substrate

Transmission line problems → Solved using EM field theory and electric circuit theory.

Transmission Line Parameters

↳ resistance per unit length R

Inductance per unit length L

Conductance per unit length G

Capacitance per unit length C

Each of lines → has specific formulas for finding R, L, G and C

For example for coaxial cable or line

$$R (\Omega/m) = \frac{1}{2\pi\delta\sigma_c} \left[\frac{1}{a} + \frac{1}{b} \right]$$

$$L (H/m) = \frac{\mu}{2\pi} \ln \frac{b}{a}$$


$$G (S/m) = \frac{2\pi\sigma}{\ln b/a}$$

$$C (F/m) = \frac{2\pi\epsilon}{\ln b/a}$$

$$\delta = \frac{1}{\sqrt{\pi f \mu_c \sigma_c}} = \text{Skin depth of the conductor}$$



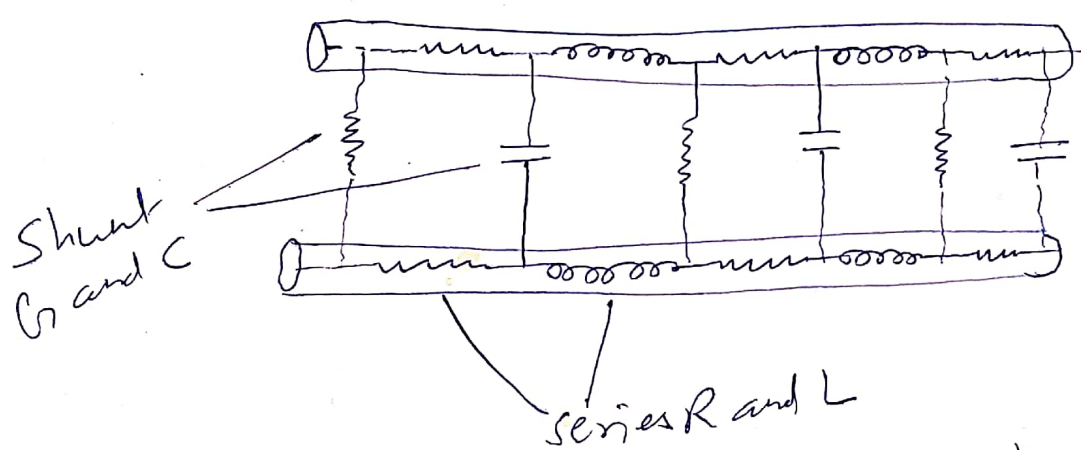1. The line parameters R, L, G and C are not discrete or lumped, parameters are uniformly distributed along the entire length of the line



2. The conductors are characterized by $\sigma_c, \mu_c, \epsilon_c = \epsilon_0$ and the homogeneous dielectric separating the conductors is characterized by σ, μ, ϵ .

3. $G \neq \frac{1}{R}$

$R \rightarrow$ ac resistance per unit length comprising the line

$G \rightarrow$ conductance per unit length due to the dielectric medium separating the conductors.


$L = L_{ext}$ external inductance per unit length

$L_{in} = \left(\frac{R}{\omega}\right) \rightarrow$ negligible at high frequencies

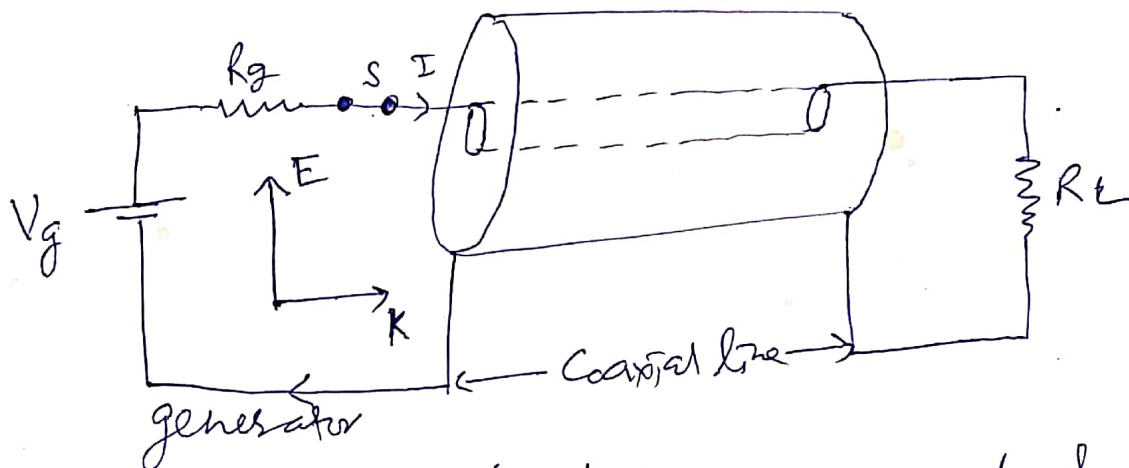5. for each line $LC = \mu \epsilon$ and $\frac{G}{C} = \frac{\sigma}{\epsilon} \quad \text{--- (1)}$


Let us consider how an EM wave ~~propagates~~ propagates through a two-conductor transmission line (27)

Consider the coaxial line connecting the generator or source to the load



When switch S is closed the inner conductor is made positive w.r.t the outer one so that the field E is radially outward

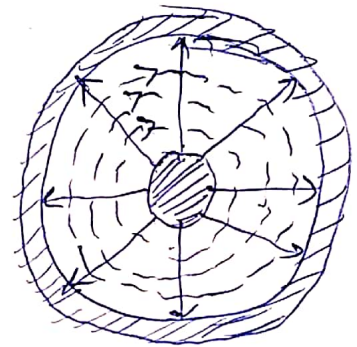According to Ampere's Law
 \rightarrow H field encircles the current carrying conductors



Poynting vector ($\underline{E} \times \underline{H}$) points along the transmission line.

\Rightarrow Closing the switch \rightarrow creates a disturbance, which appears as a transverse electromagnetic (TEM) wave propagating along the line.

Transmission Line Equations

A two conductor transmission line supports a TEM wave i.e. electric and magnetic fields on the line are transverse to the direction of wave propagation.


for a TEM wave \rightarrow fields E and H are uniquely related to V and I respectively

$$V = - \int E \cdot dl, \quad I = \oint H \cdot dl \quad \dots (2)$$

We use circuit quantities V and I in solving the transmission line problem

We examine an incremental portion of length Δz of a two-conductor transmission line

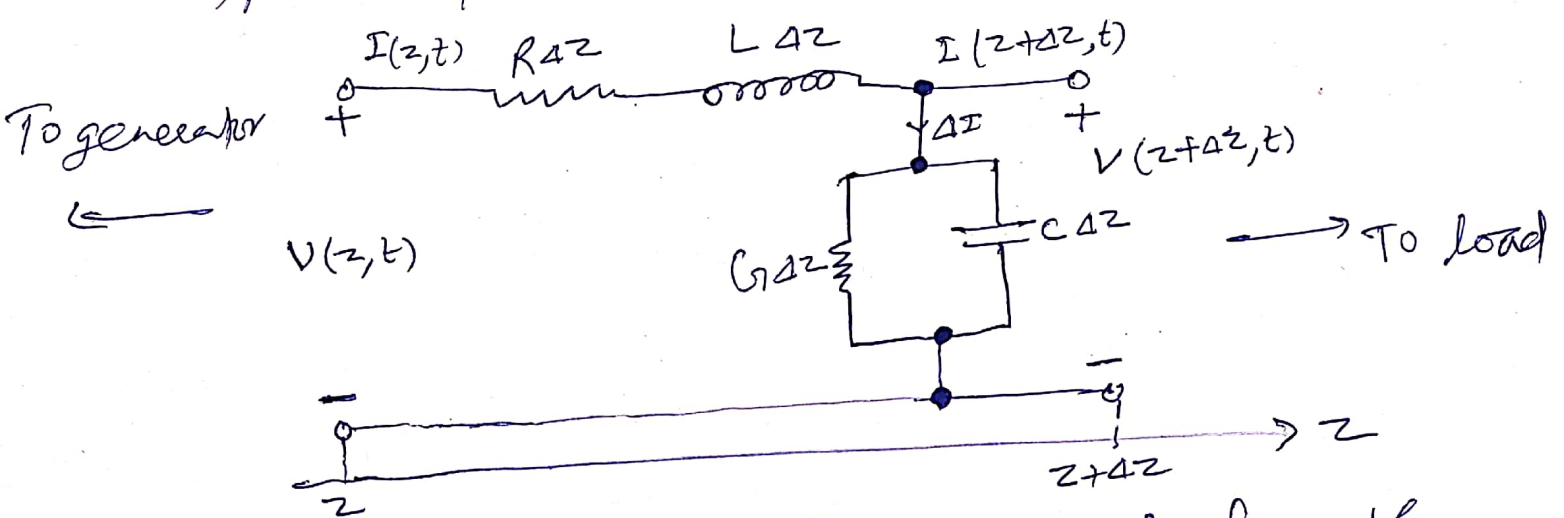We take an equivalent circuit, called the ~~TL~~ L-type equivalent circuit



Wave propagates along the $+z$ direction from the generator to the load.

By applying Kirchhoff's voltage law to the outer loop (29) of the circuit

$$V(z, t) = R \Delta z I(z, t) + L \Delta z \frac{\partial I(z, t)}{\partial t} + V(z + \Delta z, t)$$

$$\text{or } \frac{V(z + \Delta z, t) - V(z, t)}{\Delta z} = R I(z, t) + L \frac{\partial I(z, t)}{\partial t} \quad \text{--- (3)}$$

as $\Delta z \rightarrow 0$

$$\frac{\partial V(z, t)}{\partial z} = R I(z, t) + L \frac{\partial I(z, t)}{\partial t} \quad \text{--- (4)}$$

Similarly, applying Kirchhoff's law to the main node of the circuit

$$\begin{aligned} I(z, t) &= I(z + \Delta z, t) + \Delta I \\ &= I(z + \Delta z, t) + G \Delta z V(z + \Delta z, t) \\ &\quad + C \Delta z \frac{\partial V(z + \Delta z, t)}{\partial t} \end{aligned}$$

$$\text{or } \frac{I(z + \Delta z, t) - I(z, t)}{\Delta z} = G V(z + \Delta z, t) + C \frac{\partial V(z + \Delta z, t)}{\partial t} \quad \text{--- (5)}$$

as $\Delta z \rightarrow 0$

$$\frac{\partial I(z, t)}{\partial z} = G V(z, t) + C \frac{\partial V(z, t)}{\partial t} \quad \text{--- (6)}$$

If we assume harmonic time dependence so that

$$V(z, t) = \text{Re} [V_s(z) e^{j\omega t}] \quad \text{--- (7a)}$$

$$I(z, t) = \text{Re} [I_s(z) e^{j\omega t}] \quad \text{--- (7b)}$$

where $V_s(z)$ and $I_s(z) \rightarrow$ phasor forms of $V(z, t)$ and $I(z, t)$ respectively